

ARDUINO 4 – MOTOR

STEVEN HAMMER


S.HAMMER@HW.AC.UK

INTRODUCTION

- Use an Arduino with PWM to control a motor
- Use a potentiometer to adjust the speed of the motor

WHAT IS PWM?

- PWM = Pulse Width Modulation

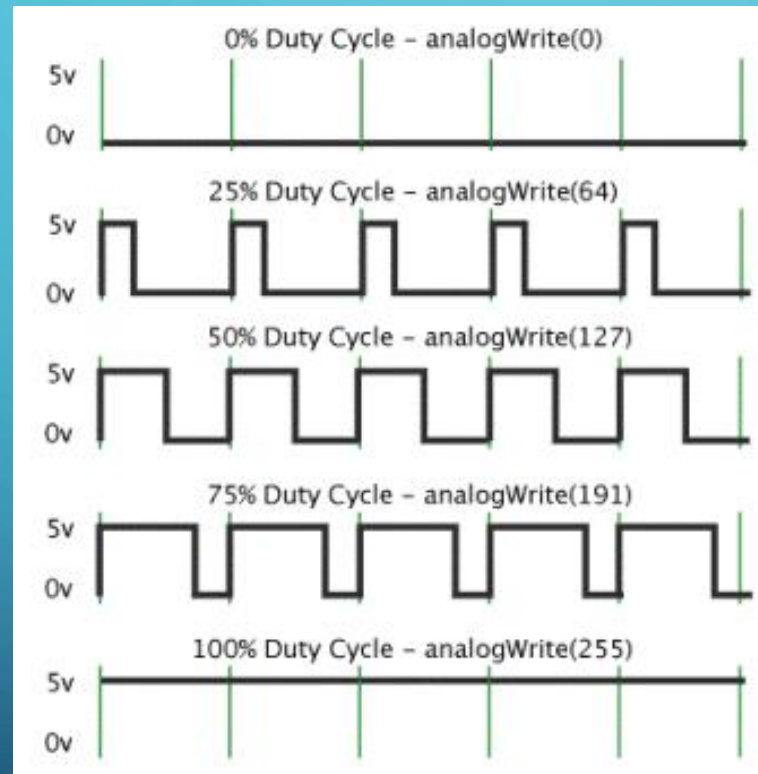


- Switch on/off at varying frequencies to control motor speed

WHAT ARE WE DOING TODAY?


1. Turn the motor on and off
2. Slowly accelerate the motor from zero to full speed then back to zero
3. Use a potentiometer to control the speed of the motor

CIRCUITS

All components included in the kit...

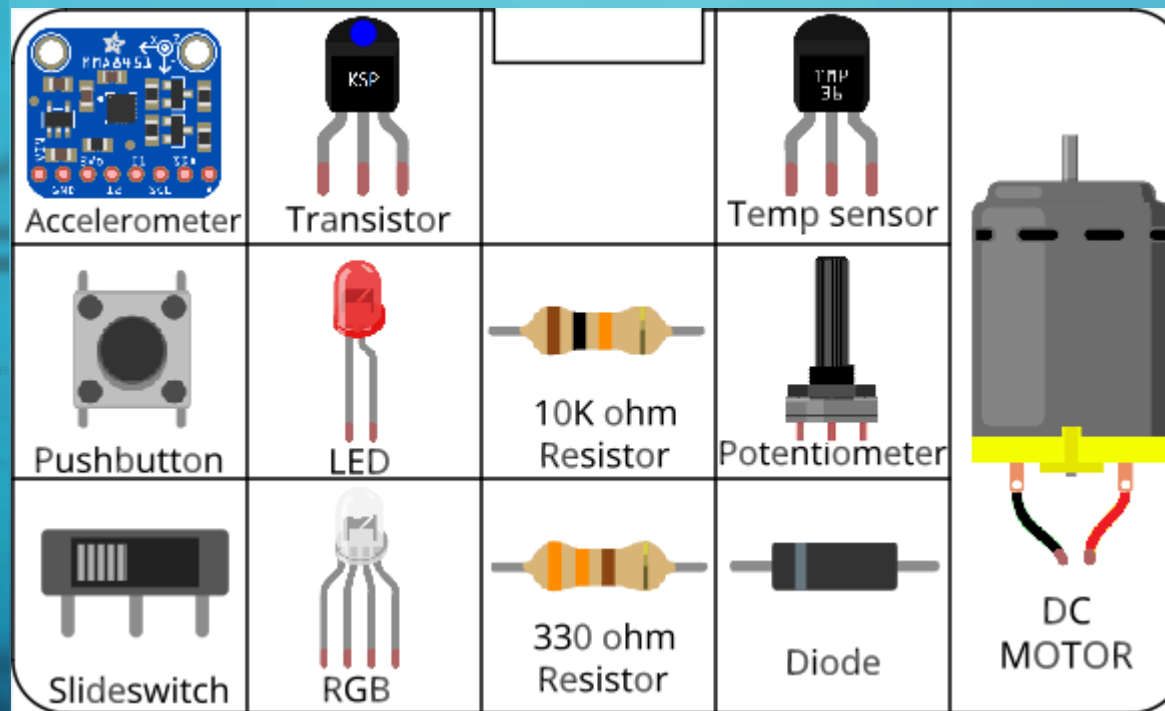


BEFORE YOU START BUILDING CIRCUITS...

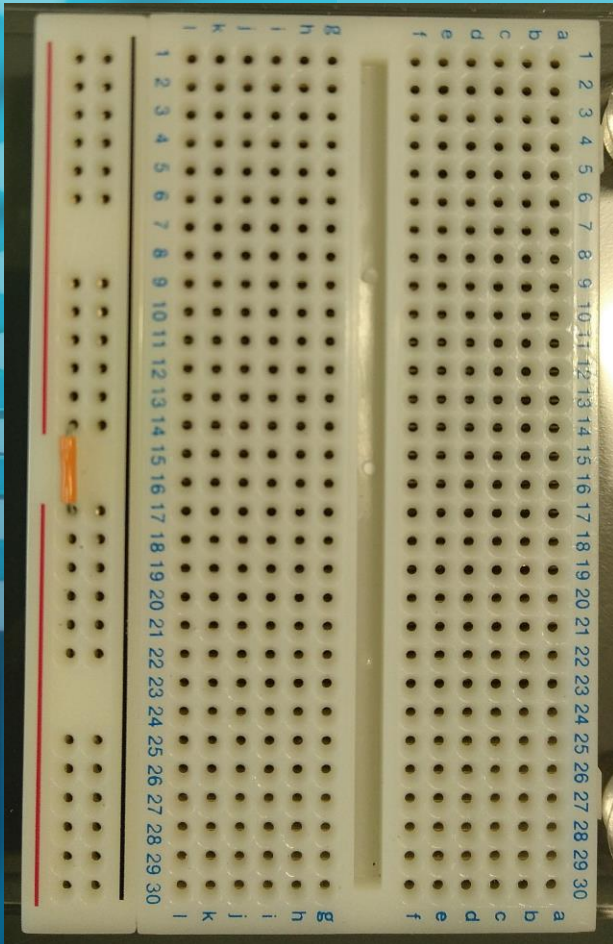

- Connect power bus (+ line) together using a small section of jumper cable

BUILDING CIRCUITS

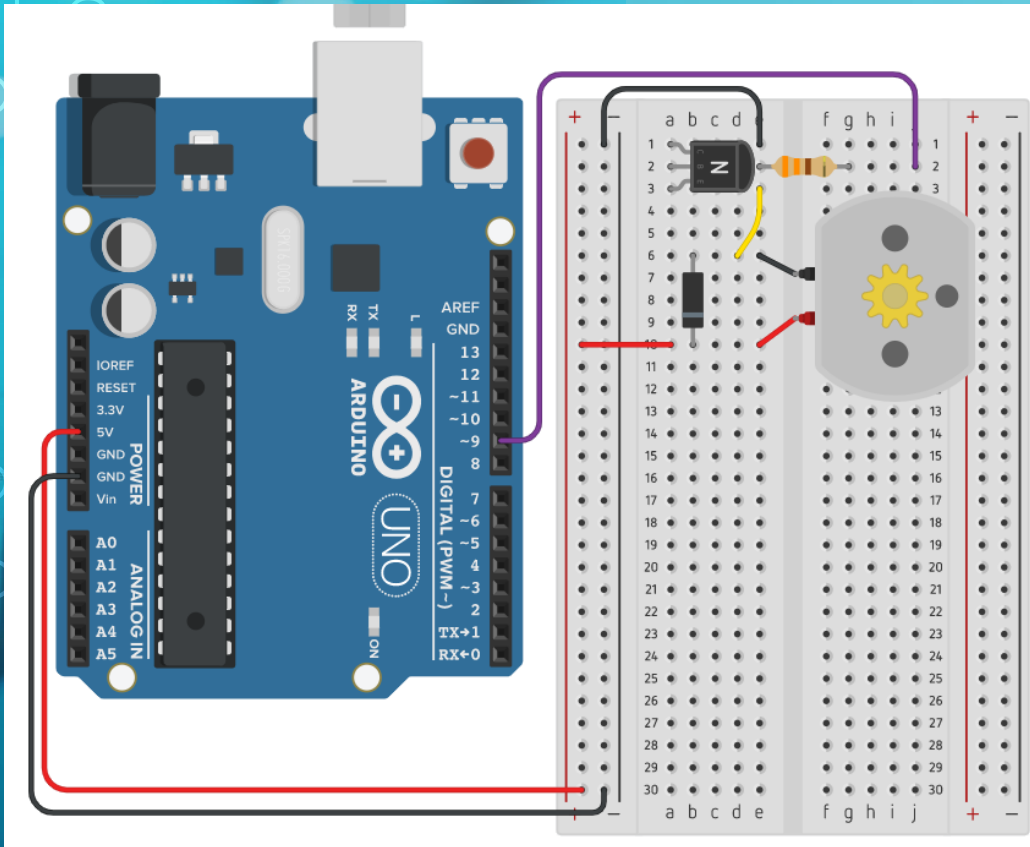

- Insert components into breadboard holes
- Connect up using instrument wire
- Arduino controls inputs and outputs
- Follow schematics

NOTE: GND = negative

DEBUGGING CODE

- Is there a space missing somewhere?
- Do all lines end with a semicolon;
- Is something commented out //

HOUSEKEEPING

- Take two boxes:
 - One Arduino box
 - One Sensors and Motion kit
- Put components back into labelled places in boxes after use
- Any components missing – let us know.

TIDYING UP

- Return components to your Sensors and Motion box
IN THE CORRECT PLACES!!!
 - Put instrument wire in motor compartment
- Return Arduino to its case
- Return both boxes to tutor

FINISHED ALREADY?

- Try the RGB LED tutorial (on Teams) if you haven't already
- Combine exercise 2 (Alarm) and this exercise:
 - Create a circuit that turns on a pump (the motor) when the low level switch is triggered on the (simulated) water tank.
 - Switch off the pump (motor) when the mid or high level is reached.